

ECE212H1F – Circuit Analysis

Lecture #15

# Second-Order Circuits

*Natural Response – Part 1*

# Second-Order Circuits:



## *General Layout*

---

- ▶ We have discussed the transient response of first-order circuits, which may include sources, resistors, and storage elements which can be reduced to a single storage element:
  
- ▶ Second-order circuits include sources, resistors, and at least two unique storage elements:

# Source-Free Series *RLC* Circuit:



## *Natural Response*

---

- ▶ Recall, the ***natural response*** of a circuit with transients relates to the release of the ***initial stored energy*** within the storage elements.
- ▶ Consider the ***series RLC*** circuit shown below. How can we find the expression for the current in the circuit for  $t > 0$ ?
  - We can use the general *differential equation approach*.
  
- ▶ If we do this (using KVL) we find that the current can be determined by solving the differential equation given by:


## Clicker

*If  $R = 0$  in the series RLC circuit shown below, what will the  $i(t)$  waveform look like?*

- A. Constant voltage
- B. Decaying exponential
- C. Growing exponential
- D. Sinusoid
- E. Damped sinusoid

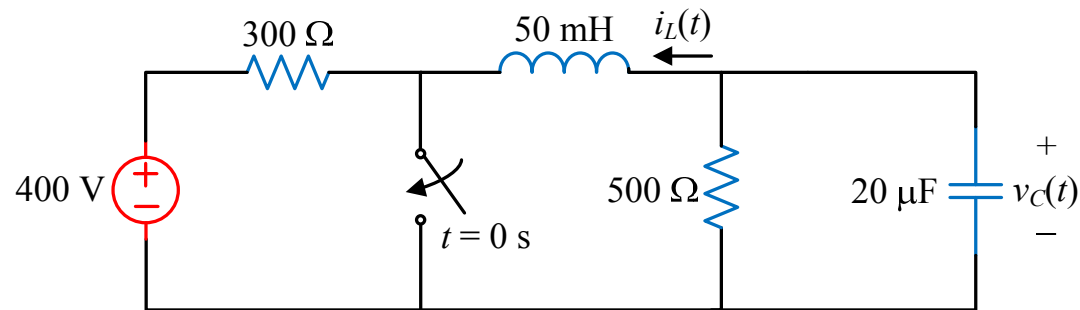
**Example:***Parallel RLC Circuit – Natural Response*

- ▶ How does the situation change if  $R$ ,  $L$ , and  $C$  are connected in parallel?
- ▶ Consider the circuit shown below. Find  $v_C(t)$  and  $i_L(t)$  for  $t > 0$ .


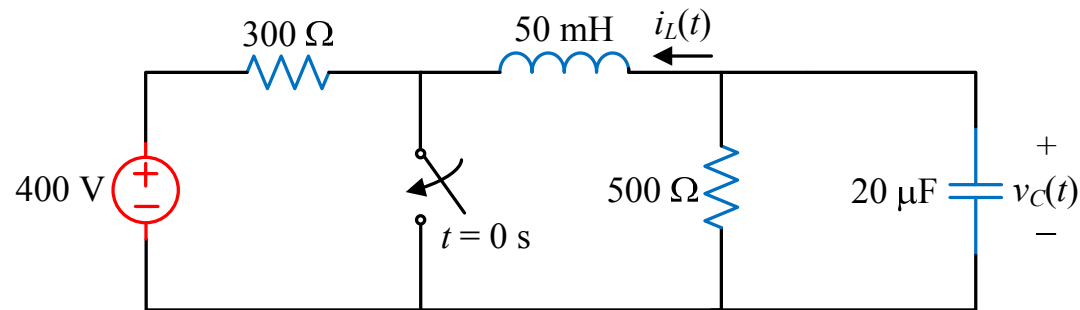
## Clicker


*For the circuit given below what is the initial value of the current through the inductor (as indicated in the circuit)?*



- A.  $i_L(0+) = 2.66$  A
- B.  $i_L(0+) = 1.33$  A
- C.  $i_L(0+) = 0.5$  A
- D.  $i_L(0+) = 0$  A
- E.  $i_L(0+) = -0.5$  A
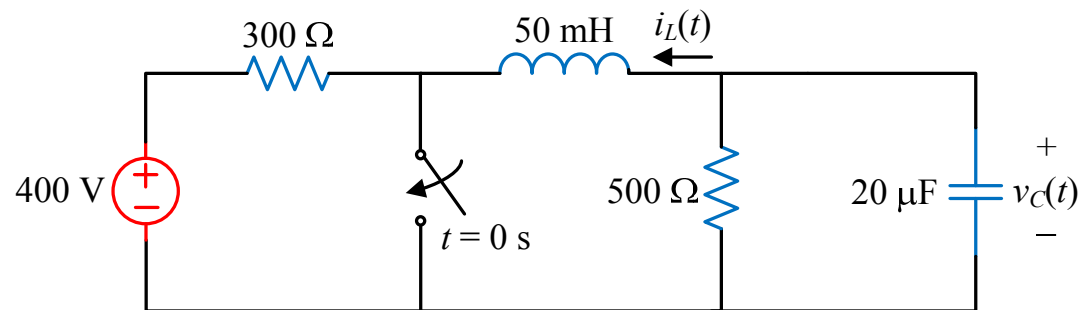
## Clicker

*For the circuit given below what is the final value of the voltage across the capacitor?*



- A.  $v_C(\infty) = 0$  V
- B.  $v_C(\infty) = 40$  V
- C.  $v_C(\infty) = 25$  V
- D.  $v_C(\infty) = 20$  V
- E.  $v_C(\infty) = -40$  V

## Example:

R G R  $\Omega$




Parallel RLC Circuit – Natural Response (cont'd)



## Example:

R G B O
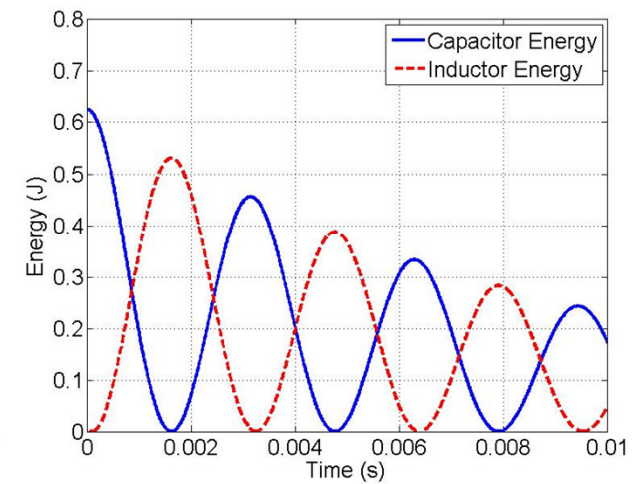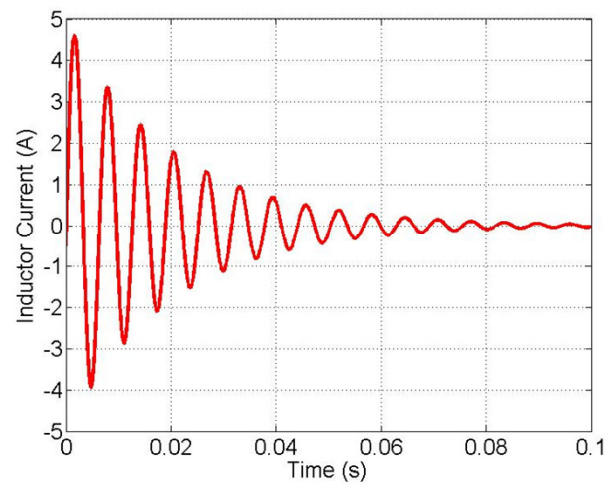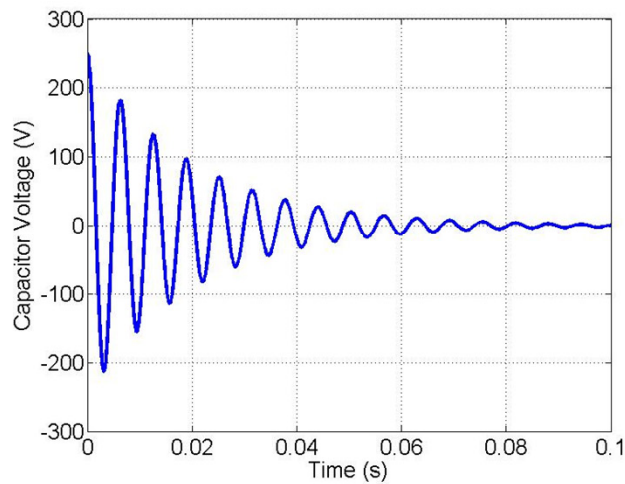
### Parallel RLC Circuit – Natural Response (cont'd)



# Second-Order Circuits:

## *Definitions*

---



- ▶ There are some important quantities which govern the response for *all* second-order circuits. These are:
- ▶ Using these we can write the general form of the differential equation which governs the ***natural response of all second-order circuits***:
- ▶ This results in the characteristic equation (auxiliary equation) of:

# Key Points

---

1. The **natural response** of a circuit relates to the situation where there is no independent source connected to the circuit after the switch moves (e.g., for  $t > 0$ )
  - ❑ This response is caused by the release of the initial energy stored in the storage elements (i.e.,  $L$ 's and  $C$ 's)
2. The final value of the natural response will always be zero due to the damping of the resistor in the circuit.
  - ❑ Meaning that all of the initial stored energy is eventually released as heat
3. The differential equation which characterizes the **natural response** of **any RLC circuit** will be homogeneous, and will have a form that looks like:

$$\frac{d^2x}{dt^2} + 2\zeta\omega_0 \frac{dx}{dt} + \omega_0^2 x = 0 \quad \text{or} \quad \frac{d^2x}{dt^2} + 2\alpha \frac{dx}{dt} + \omega_0^2 x = 0$$

4. The **solution to this differential equation** can be found by finding the roots of the characteristic equation, i.e.,  $m_1, m_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
5. The basic quantities are:  $\omega_0$  = undamped natural frequency,

$\alpha$  = damping factor,

$\zeta$  = damping ratio, and

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  damped natural frequency.

# Key Points

---

6. For general *RLC* circuits, the way in which these basic quantities relate to the circuit elements *R*'s, *L*'s, and *C*'s, depend on the how that circuit is connected.
7. If the circuit has a **series RLC** connection circuits the roots are  $m_1, m_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$  and the basic quantities are
  - Undamped natural frequency =  $\omega_0 = \frac{1}{\sqrt{LC}}$
  - Damping factor =  $\alpha = \frac{R}{2L}$
  - Damping ratio =  $\zeta = \frac{\alpha}{\omega_0}$
8. If the circuit has a **parallel RLC** circuits the are  $m_1, m_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$ , and the basic quantities are
  - Undamped natural frequency =  $\omega_0 = \frac{1}{\sqrt{LC}}$
  - Damping factor =  $\alpha = \frac{1}{2RC}$
  - Damping ratio =  $\zeta = \frac{\alpha}{\omega_0}$
9. In the expressions for the series and parallel *RLC* circuits, the ***R* is the total resistance that the storage elements “see”** (for example, this is the total resistance that the *L* and *C* are in series with, or the total resistance that the *L* and the *C* are in parallel with)